

BCD Counter

Nathanial Hendler

June 17, 2009

Abstract

Designing a simple, but human friendly digital counter can present several problems for an Engineer to overcome. Here a circuit is designed around discrete logic ICs, 7-segment displays and a rotary telephone dial to explore these issues.

1 Introduction

Traditionally digital circuits count in binary, a numbering system foreign to the average person. Engineers are required to create solutions in software or hardware to convert the binary to decimal, or base ten, a system familiar and useful to the everyday person. However, a third option exists: counting in binary coded decimal.

A digital counter was designed using TTL logic chips, a rotary telephone dial as an input and a pair of 7-segment displays for output to tackle this, and few other peripheral digital design issues, for the purpose of hands-on-learning.

2 Design Challenges

2.1 Roll-Your-Own Carry

Table 1 or in Figure 1, blah blah blah.

$$V_{pin} = V_{cc}[1 - e^{(-t/\tau)}] \quad (1)$$

D	C	B	A	X
0	0	0	0	0
0	0	0	1	0
		...		0
1	0	0	1	0
1	0	1	0	1

Table 1: Binary greater than nine truth table.

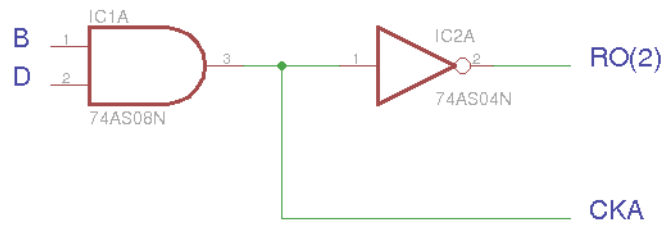


Figure 1: Resulting logic from truth table.

$$\tau = RC = 10k\Omega \underbrace{(C_1 \parallel C_2)}_{20nF} = 5ms \quad (2)$$